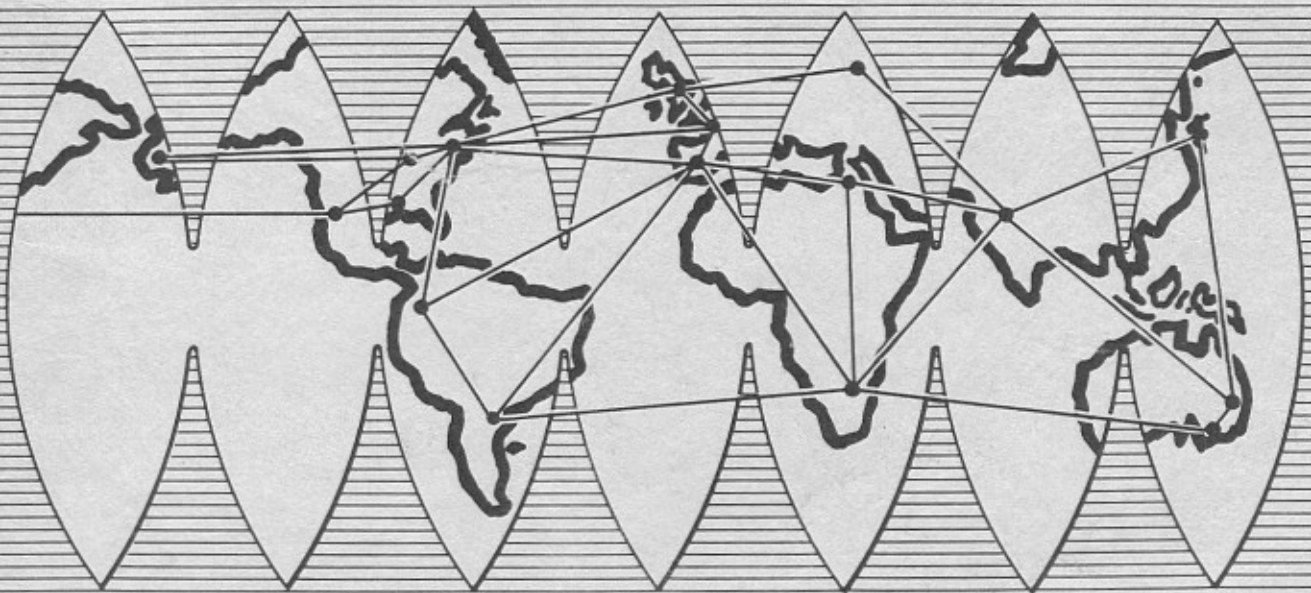


NCR

**Data
Communications
Concepts**



Basic Concepts Manual

DATA COMMUNICATIONS CONCEPTS

CONTENTS

VERBAL AND VISUAL COMMUNICATIONS	Sec. A	THE DECIBEL, A RATIO OF POWERS	Sec. 1
VERBAL COMMUNICATION PROBLEMS	A-1	WIRE GAUGES	App. 14
VISUAL COMMUNICATION PROBLEMS	A-2	CENTURY ONLINE EQUIPMENT	App. 15
SUMMARY	A-3	COMMON LOGARITHMS	App. 16
DATA COMMUNICATIONS CONCEPTS			
COMPUTERS AND COMMUNICATIONS	Sec. B	DC-ORGE CONVERSION CHART	App. 17
SIMPLE MECHANICAL COMPUTERS	B-1	STANDARD INTERFACE CONNECTIONS	App. 18
ELECTRONIC COMPUTERS	B-2	NATIONAL TELETYPE	App. 19
COMPUTER COMMUNICATIONS	B-3	ALPHABET NO. 2	App. 20
COMPUTERS AND COMMUNICATIONS AT NCR	B-4	RATIO TO DB QUICK CONVERSION CHART	App. 21
SUMMARY	B-5	REFERENCE FORMULAS	App. 22
TELEPHONE SYSTEMS	Sec. C	GLOSSARY OF EDP-COMMUNICATIONS TERMS	App. 23
DIRECT TELEPHONE SYSTEMS	C-1	ANSWERS TO QUESTIONS	App. 24
SWITCHED TELEPHONE SYSTEMS	C-2		
TELEPHONE COMPANIES AND REGULATIONS	C-3		
SUMMARY	C-4		
CIRCUIT TERMINATIONS AND MODES OF OPERATION	Sec. D		
COMMUNICATIONS CIRCUITS	D-1		
MODES OF OPERATION	D-2		
DEDICATED LINES	D-3		
SUMMARY	D-4		
CONVENTIONAL INTELLIGENCE SIGNALS	Sec. E		
WAVE CHARACTERISTICS	E-1		
BANDS AND BANDWIDTH	E-2		
WIRE TRANSMISSION	E-3		
COAXIAL TRANSMISSION	E-4		
WAVE TYPE TRANSMISSION	E-5		
DATA TRANSMISSION	E-6		
TRANSMISSION RATES	E-7		
SUMMARY	E-8		
MODULATION METHODS AND TECHNIQUES	Sec. F		
CARRIERS AND MODULATION	F-1		
AMPLITUDE MODULATION	F-2		
FREQUENCY MODULATION	F-3		
SINGLE SIDEBAND	F-4		
FREQUENCY SHIFT KEYING	F-5		
EDP TECHNICIANS AND TRANSMISSION PROBLEMS	F-6		
SUMMARY	F-7		
BASIC CARRIER SYSTEMS	Sec. G		
TIME DIVISION MULTIPLEXING	G-1		
FREQUENCY DIVISION MULTIPLEXING	G-2		
GROUPS, SUPERGROUPS, AND MASTERGROUPS	G-3		
SYSTEMS USING THE PUBLIC SWITCHED NETWORK	G-4		
SUMMARY	G-5		
BASIC CHARACTERISTICS OF A WIRE TRANSMISSION LINE	Sec. H		
RESISTANCE	H-1		
REACTANCE	H-2		
IMPEDANCE	H-3		
WAVELENGTH	H-4		
SUMMARY	H-5		
INTERPRETING CIRCUIT SPECIFICATIONS	Sec. I		
SELECTING A SERVICE	I-1		
CIRCUIT DESIGNATIONS	I-2		
GENERAL CHARACTERISTICS	I-3		
ATTENUATION CHARACTERISTICS	I-4		
DELAY CHARACTERISTICS	I-5		
NOISE CHARACTERISTICS	I-6		
SUMMARY	I-7		
MODEMS IN DATA TRANSMISSION	Sec. J		
BASIC MODEM CHARACTERISTICS	J-1		
MODES OF OPERATION	J-2		
WIRE MODEM	J-3		
PROBLEMS AND TROUBLESHOOTING	J-4		
SUMMARY	J-5		
REFERENCE DATA	App. 1		
ALPHABETIC CODE CHART AND ABBREVIATIONS	App. 2		
WIRE GAUGES	App. 3		
CENTURY ONLINE EQUIPMENT	App. 4		
COMMON LOGARITHMS	App. 5		
DC-ORGE CONVERSION CHART	App. 6		
STANDARD INTERFACE CONNECTIONS	App. 7		
NATIONAL TELETYPE	App. 8		
ALPHABET NO. 2	App. 9		
RATIO TO DB QUICK CONVERSION CHART	App. 10		
REFERENCE FORMULAS	App. 11		
GLOSSARY OF EDP-COMMUNICATIONS TERMS	App. 12		
ANSWERS TO QUESTIONS	App. 13		

Prepared by
 Technical Publications Department
 Marketing Education and Publications Division

Copyright © 1971
 The National Cash Register Company
 Dayton, Ohio, United States of America
 All Rights Reserved
 Printed in U.S.A.

MS-826

Revised January 15, 1975

BASIC
 CONCEPTS
 MANUAL

DATA COMMUNICATIONS CONCEPTS

CONTENTS

<p>VERBAL AND VISUAL COMMUNICATIONS Sec. A VERBAL COMMUNICATION PROCESSES A-1 VISUAL COMMUNICATION PROCESSES A-2 SUMMARY A-2</p> <p>COMPUTERS AND COMMUNICATIONS Sec. B SIMPLE MECHANICAL COMPUTERS B-1 ELECTRONIC COMPUTERS B-1 COMPUTER COMMUNICATIONS B-2 COMPUTERS AND COMMUNICATIONS AT NCR B-2 SUMMARY B-3</p> <p>TELEPHONE SYSTEMS Sec. C DIRECT TELEPHONE SYSTEMS C-1 SWITCHED TELEPHONE SYSTEMS C-1 TELEPHONE COMPANIES AND REGULATIONS C-2 SUMMARY C-2</p> <p>CIRCUIT TERMINATIONS AND MODES OF OPERATION Sec. D COMMUNICATIONS CIRCUITS D-1 MODES OF OPERATION D-1 DEDICATED LINES D-2 SUMMARY D-2</p> <p>CONVENTIONAL INTELLIGENCE SIGNALS Sec. E VOICE CHARACTERISTICS E-1 BANDPASS AND BANDWIDTH E-1 VOICE TRANSMISSION E-1 FACSIMILE TRANSMISSION E-2 TELETYPE TRANSMISSION E-3 DATA TRANSMISSION E-4 TRANSMISSION RATES E-4 SUMMARY E-5</p> <p>MODULATION METHODS AND TECHNIQUES Sec. F CARRIERS AND MODULATION F-1 AMPLITUDE MODULATION F-1 FREQUENCY MODULATION F-2 SINGLE SIDEBAND F-3 FREQUENCY SHIFT KEYING F-4 EDP TECHNICIANS AND TRANSMISSION PROBLEMS F-6 SUMMARY F-6</p> <p>BASIC CARRIER SYSTEMS Sec. G TIME DIVISION MULTIPLEXING G-1 FREQUENCY DIVISION MULTIPLEXING G-1 GROUPS, SUPERGROUPS, AND MASTERGROUPS G-2 SYSTEMS USING THE PUBLIC SWITCHED NETWORK G-4 SUMMARY G-5</p> <p>BASIC CHARACTERISTICS OF A WIRE TRANSMISSION LINE Sec. H RESISTANCE H-1 REACTANCE H-2 IMPEDANCE H-2 IMPEDANCE MATCHING H-3 SUMMARY H-4</p>	<p>THE DECIBEL, A RATIO OF POWERS Sec. I BELS I-1 LOGARITHMIC NOTATION I-2 DETERMINING THE LOGARITHM OF A NUMBER I-2 DECIBEL CASE STUDIES I-4 SUMMARY I-5</p> <p>A SURVEY OF TRANSMISSION PROBLEMS Sec. J ATTENUATION J-1 NOISE J-2 CROSSTALK J-4 ECHOES AND REFLECTIONS J-4 DELAY J-5 OTHER TRANSMISSION PROBLEMS J-9 SUMMARY J-9</p> <p>CORRECTIVE ELEMENTS IN TELEPHONE CIRCUITS Sec. K AMPLIFIERS K-1 IMPEDANCE MATCHING DEVICES K-2 FILTERS K-3 EQUALIZERS K-4 ECHO SUPPRESSORS K-5 COMPANDERS K-5 SUMMARY K-6</p> <p>INTERPRETING CIRCUIT SPECIFICATIONS Sec. L SELECTING A SERVICE L-1 CIRCUIT DESIGNATIONS L-1 GENERAL CHARACTERISTICS L-1 ATTENUATION CHARACTERISTICS L-2 DELAY CHARACTERISTICS L-2 NOISE CHARACTERISTICS L-3 SUMMARY L-3</p> <p>MODEMS IN DATA TRANSMISSION Sec. M BASIC MODEM CHARACTERISTICS M-1 MODES OF OPERATION M-2 REVERSE CHANNEL M-3 MODEM TESTING AND TROUBLESHOOTING M-4 SUMMARY M-6</p> <p>REFERENCE DATA App. I USASCII CODE CHART AND ABBREVIATIONS App. I-3 WIRE GAUGES App. I-4 CENTURY ONLINE EQUIPMENT App. I-5 COMMON LOGARITHMS App. I-7 DB QUICK CONVERSION CHART App. I-9 STANDARD INTERFACE CONNECTIONS App. I-10 INTERNATIONAL TELETYPE ALPHABET NO. 2 App. I-11 RATIO-TO-DB QUICK CONVERSION CHART App. I-12 REFERENCE FORMULAS App. I-13</p> <p>GLOSSARY OF EDP-COMMUNICATIONS TERMS App. II</p> <p>ANSWERS TO QUESTIONS App. III</p>
--	---

ILLUSTRATIONS

Voice-communication process	A-2	Effect of attenuation on FSK waveforms	J-1
Abacus	B-1	Theoretical frequency response graph	J-1
Central processing unit block diagram	B-1	Effect of attenuation distortion	J-1
Functional elements of a computer system	B-2	Effect of high frequency attenuation distortion	J-2
Present "online" concept	B-2	Circuit for random noise measurement	J-3
Disadvantage of direct connections	C-1	Equivalence of dbm and dbrnC measurements	J-3
A telephone exchange	C-1	Signal-plus-noise waveform	J-3
Exchange and toll system	C-2	Noise waveform showing impulse noise	J-4
Full-duplex mode of operation	D-1	Crosstalk in a multiconductor cable	J-4
Balanced and unbalanced terminations	D-1	Effect of impedance mismatch	J-5
Public versus dedicated (private) lines	D-2	Theoretical transmission line	J-5
Two configurations of online systems	D-2	1000-Hz waveforms	J-5
Bandwidth and bandpass comparison	E-1	A dispersive medium	J-7
Basic principles of voice transmission	E-2	Typical phase velocity versus frequency curve	J-7
Representation of a facsimile signal	E-2	Phase shift curve (typical)	J-7
Elements of a teletype transmission system	E-3	Envelope delay curve	J-7
Letter "P" in international teletype alphabet number 2	E-3	Envelope delay measurement methods	J-8
Representative point-to-point online system	E-4	Lissajous display of phase differences	J-8
One character of ASCII code: the letter "P"	E-4	Lissajous patterns	J-8
Amplitude modulation frequency relationships	F-1	Eye pattern	J-9
Waveforms of amplitude-modulated signals	F-2	Jitter of a data waveform	J-9
Difference between linear and nonlinear mixers	F-2	Amplifier circuit and symbol	K-1
AM demodulator waveforms	F-2	Amplifier installation in transmission lines	K-1
Frequency-modulated waveforms	F-3	Signal power level versus noise power level diagram	K-1
Deviation of the FM carrier frequency from center	F-3	A 4-wire repeater	K-1
Generating a single-sideband (SSB) signal	F-3	A 2-wire repeater	K-2
Common method of generating SSB signals	F-4	Terminal repeater	K-2
Demodulation of single sideband signals	F-4	Transformer balanced to unbalanced connections	K-2
Frequency shift keyed waveforms	F-4	Use of transformers for circuit isolation	K-2
Location of FSK frequencies within the voice channel	F-5	Bridging transformer connections	K-3
Simple method of generating FSK	F-5	Common pad circuits	K-3
A more conventional method of producing FSK	F-5	High-pass "L" type filter	K-3
Filter method of FSK demodulation	F-5	Low-pass "T" type filter	K-3
A basic multiplex system	G-1	Complex bandpass filter	K-3
Time-division multiplexing and demultiplexing	G-1	Complex band-reject filter	K-4
Changing the location of an information channel	G-1	Weighting curves	K-4
Generating the four channels of a pregroup	G-2	Basic amplitude equalizer circuit	K-4
Location of channels in a pregroup	G-2	Function of equalizer-amplifier circuits	K-4
Forming a group	G-3	Delay equalizer response	K-5
Locating one channel in a mastergroup	G-3	Echo effect in 2-to-4-wire converters	K-5
Demultiplexing a mastergroup into supergroups	G-3	Echo-suppressor location in toll and carrier systems	K-5
Demultiplexing a supergroup into groups	G-3	Echo-suppressor basic functions	K-5
Demultiplexing a group into pregroups	G-4	Basic circuit using companders	K-5
Demultiplexing a pregroup into original voice channels	G-4	Effect of companders in a communications circuit	K-5
Carrier system capabilities	G-4	Normal attenuation characteristic	L-2
Example of line resistance effect	H-1	Expected variations in channel attenuation	L-2
Representation of inductance in line sections	H-2	Basic MODEM block diagram	M-1
Graphing inductive reactance	H-2	Control signal functional diagram	M-2
Representation of capacitance in line sections	H-2	Data-signal formats, synchronous and asynchronous modes	M-2
Graphing capacitive reactance	H-2	Basic reverse channel concept	M-3
Impedance factors of wired transmission lines	H-3	Location of the reverse and data channels	M-3
Typical impedance/frequency curve for cable	H-3	Combining the reverse and forward channels	M-4
Impedance matched circuit	H-4	Local-test mode	M-4
Intentional mismatched impedances	H-4	Remote-test mode	M-5
Gain in power and db	I-1	Sample MODEM block diagram and test points	M-5
Circuit for decibel calculations	I-3	Relationship between a.c. waveform values	I-3
CCITT speeds and frequencies	F-6	Table of equivalence (dbm)	I-4
Two-state representations	F-6	Examples of absolute delay	J-6
Relative resistance of some common metals	H-1	Typical circuit noise objective	L-3
Some common wire sizes	H-1	Parallel-transfer frequencies	M-3
Bels as power ratios, gains, and losses	I-1	Test point indications	M-5
Integral part of common logarithms	I-2		

TABLES